



## Computer Architecture Lab #2

### Objectives

After this lab, the student should:

- Understand VHDL basics:
  - Multiple Architectures for same entity
  - Generic Entities
  - Use of (For ... Generate)
  - Understand (When ... Else) VS (With ... Select)

### Requirements

Design a n-bit ALSU that accepts two n-bit input values A and B and provides output F, the ALSU has 4 selection inputs S<sub>3</sub>, S<sub>2</sub>, S<sub>1</sub>, S<sub>0</sub> and Cin input. The ALSU provides a total of 20 operations specified in the following table

	S <sub>3</sub>	S <sub>2</sub>	S <sub>1</sub>	S <sub>0</sub>	Cin = 0	Cin = 1
Part A	0	0	0	0	F = A	F = A + 1
	0	0	0	1	F = A + B	F = A + B + 1
	0	0	1	0	F = A - B - 1	F = A - B
	0	0	1	1	F = A - 1	F = 0
Part B	0	1	0	0	Done Last Lab	
	0	1	0	1		
	0	1	1	0		
	0	1	1	1		
Part C	1	0	0	0		
	1	0	0	1		
	1	0	1	0		
	1	0	1	1		
Part D	1	1	0	0		
	1	1	0	1		
	1	1	1	0		
	1	1	1	1		

Deliverables :

1. Write VHDL code for part A in a separate VHDL files (don't forget to output the carry out)
2. You should use the full-adder given in the explanation instead of the VHDL operators (+) and (-)
3. Compile, your Code should be free of errors and warnings.
4. Simulate partA using Do file (**TestCases at the end of the Document**).
5. **Bonus** : optimized design (hint: you can use one full adder for part A).
6. **Assignment**: Integrate the 4 parts in one file And Make all of them **Generic and Simulate them using Do file**.

**N.B. you will be graded for code neatness and understanding, Good luck**



To test part A use the following table, let n = 16

Operation	A	B	Cin	Cout	F
F = A	0F0F	-	0	0	0F0F
F = A + B	0F0F	0001	0	0	0F10
	FFFF	0001	0	1	0000
F = A - B - 1	FFFF	0001	0	1	FFFD
F = A - 1	FFFF	-	0	1	FFFE
F = A + 1	0F0E	-	1	0	0F0F
F = A + B + 1	FFFF	0001	1	1	0001
F = A - B	0F0F	0001	1	1	0F0E
F = 0	-	-	1	0	0000

To Test the Assignment

Operation	A	B	Cin	Cout	F
F = A	0F0F	-	0	0	0F0F
F = A + B	0F0F	0001	0	0	0F10
	FFFF	0001	0	1	0000
F = A - B - 1	FFFF	0001	0	1	FFFD
F = A - 1	FFFF	-	0	1	FFFE
F = A + 1	0F0E	-	1	0	0F0F
F = A + B + 1	FFFF	0001	1	1	0001
F = A - B	0F0F	0001	1	1	0F0E
F = 0	-	-	1	0	0000

  

Operation	A	B	F	Operation	A	Cin	F
AND	0F0F	000A	000A	F=Rotate right A with Carry	0F0F	0	0787
OR	0F0F	000A	0F0F	F=Rotate right A with Carry	0F0F	1	8787
XOR	0F0F	000A	0F05	F=Logic shift left A	0F0F	-	1E1E
NOT	0F0F	-	F0F0	F=Rotate left A	F0F0	-	E1E1
F=Logic shift right A	0F0F	-	0787	F=Rotate left A with Carry	F0F0	0	E1E0
F=Rotate right A	0F0F	-	8787	F=Rotate left A with Carry	F0F0	1	E1E1
F=0000	-	-	0000	F=Arithmetic shift right A	F0F0	-	F878